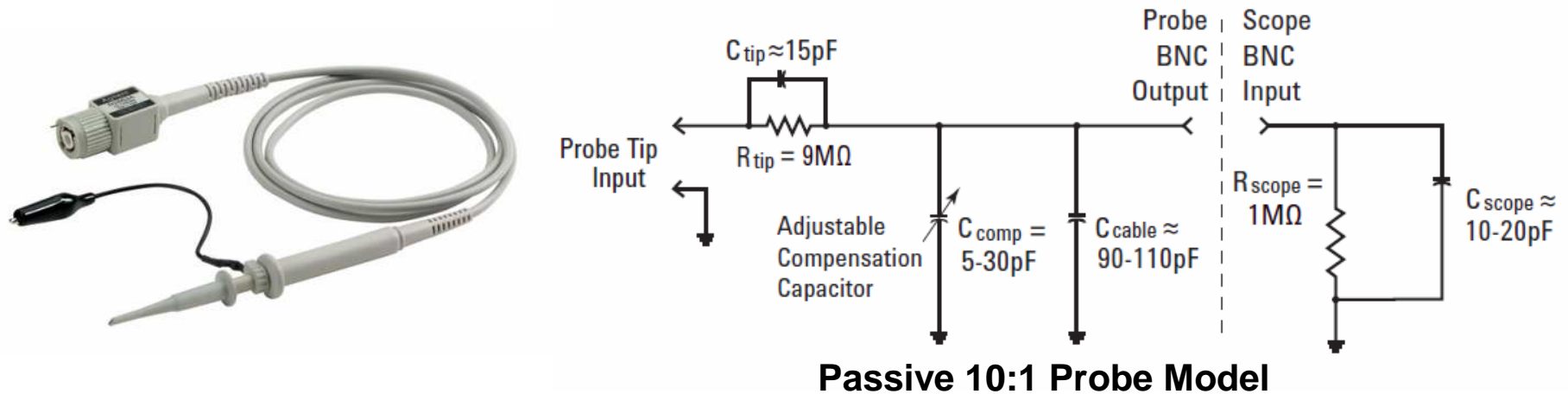


Probing Basics

- Probes are used to transfer the signal from the device-under-test to the oscilloscope's BNC inputs.
- There are many different kinds of probes used for different and special purposes (high frequency applications, high voltage applications, current, etc.).
- The most common type of probe used is called a "Passive 10:1 Voltage Divider Probe".



Passive 10:1 Voltage Divider Probe



Passive: Includes no active elements such as transistors or amplifiers.


10-to-1: Reduces the amplitude of the signal delivered to the scope's BNC input by a factor of 10. Also increases input impedance by 10X.

Note: All measurements must be performed relative to ground!



Agilent Technologies

Probing Revisited - Dynamic/AC Probe Model

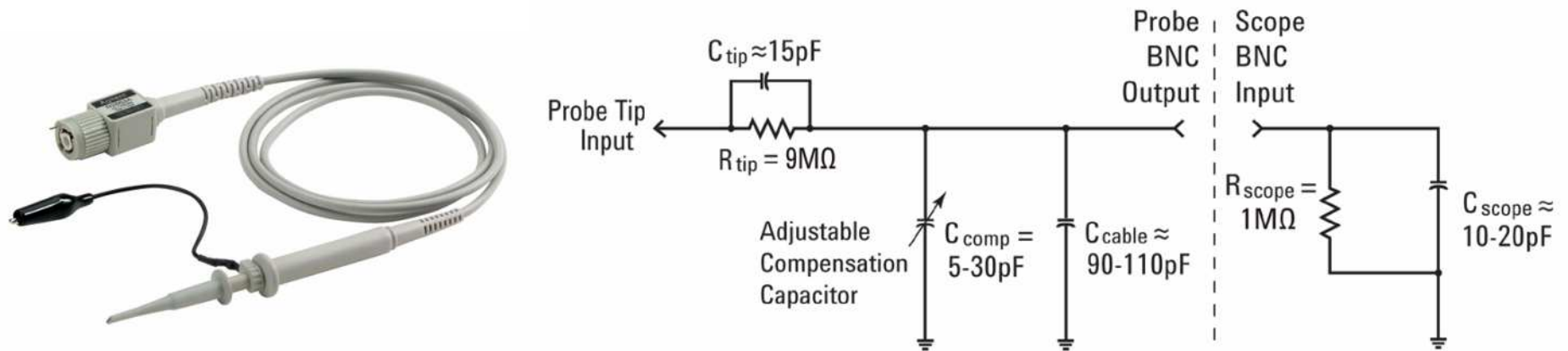

Passive 10:1 Probe Model


- C_{scope} and C_{cable} are inherent/parasitic capacitances (not intentionally designed-in)
- C_{tip} and C_{comp} are intentionally designed-in to compensate for C_{scope} and C_{cable} .
- With properly adjusted probe compensation, the dynamic/AC attenuation due to frequency-dependant capacitive reactances should match the designed-in resistive voltage-divider attenuation (10:1).

$$\frac{1}{2\pi f C_{tip}} = \frac{9}{2\pi f C_{parallel}}$$

Where $C_{parallel}$ is the parallel combination of $C_{comp} + C_{cable} + C_{scope}$



Compensating the Probes

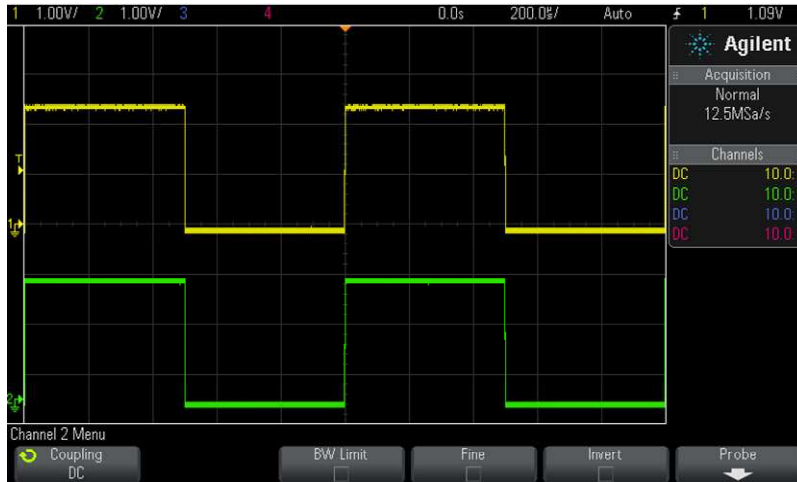

Proper Compensation




**Channel-1 (yellow) = Over compensated
Channel-2 (green) = Under compensated**

- Connect Channel-1 and Channel-2 probes to the “Probe Comp” terminal (same as Demo2).
- Adjust V/div and s/div knobs to display both waveforms on-screen.
- Using a small flat-blade screw driver, adjust the variable probe compensation capacitor (C_{comp}) on both probes for a flat (square) response.

Probe Loading

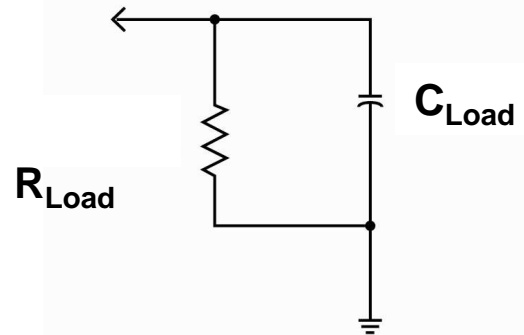- The probe and scope input model can be simplified down to a single resistor and capacitor.



Probe + Scope Loading Model

- Any instrument (not just scopes) connected to a circuit becomes a part of the circuit under test and will affect measured results... especially at higher frequencies.
- “Loading” implies the negative affects that the scope/probe may have on the circuit’s performance.

